

System Design functional Decomposition
EchoKeys 49

Alex Alexander, Jonathan Knapp, Jorge Sandoval, and Nick Stites

Department of Electrical and Computer Engineering, Portland State University


ECE 411: Industry Design Processes

Andrew Greenberg

November 10th, 2025




Level 0:

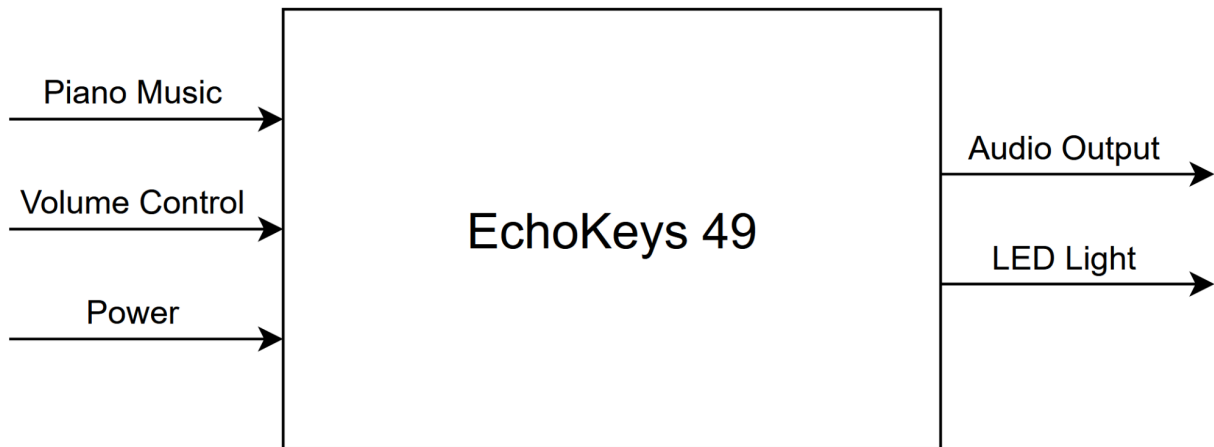


<i>Module</i>	EchoKeys 49 ~ “49 keys, mirrored in light.”
<i>Inputs</i>	• Piano Music: 0.5V peak • Volume Control: variable • Power: plugged into wall; 120V AC, 60Hz
<i>Outputs</i>	• Audio output • LED lights
<i>Functionality</i>	Take incoming piano music (500 mV max) and play the music through a speaker (variable) while showing which keys are being played.

Level 1:

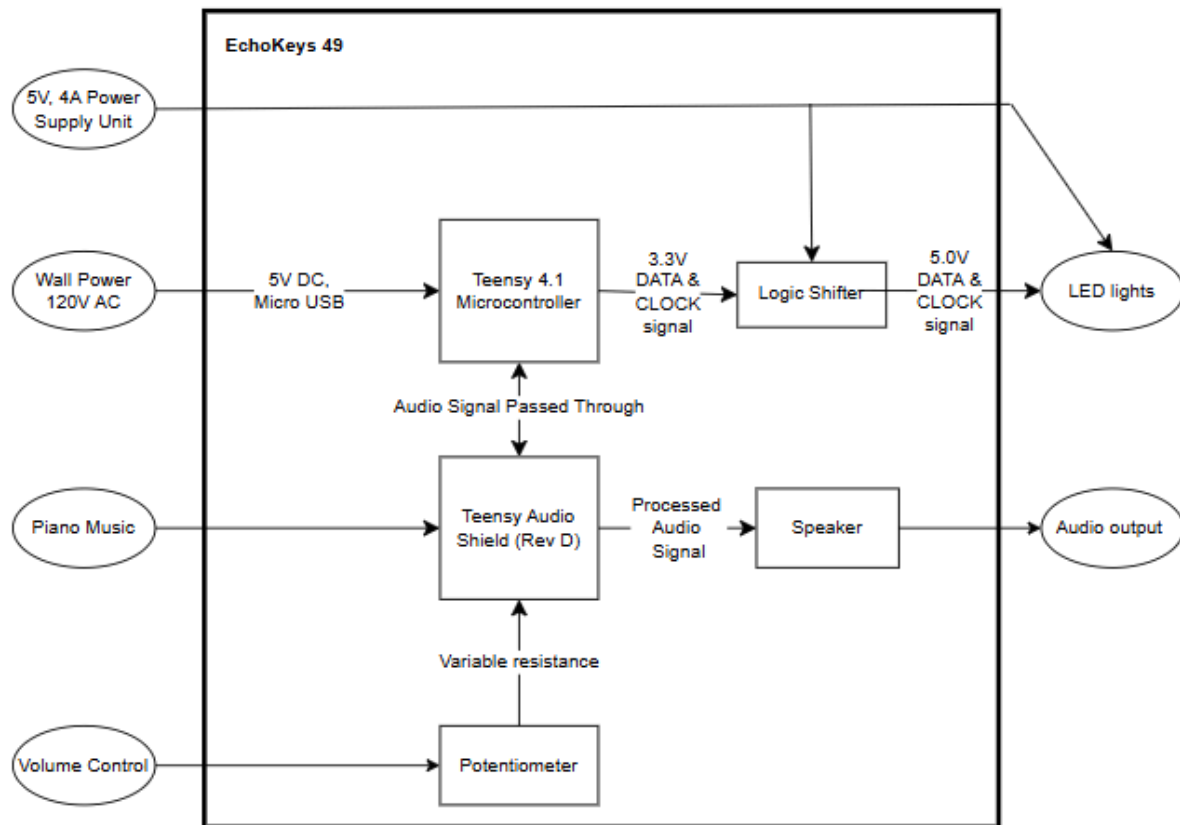


Teensy 4.1 Microcontroller

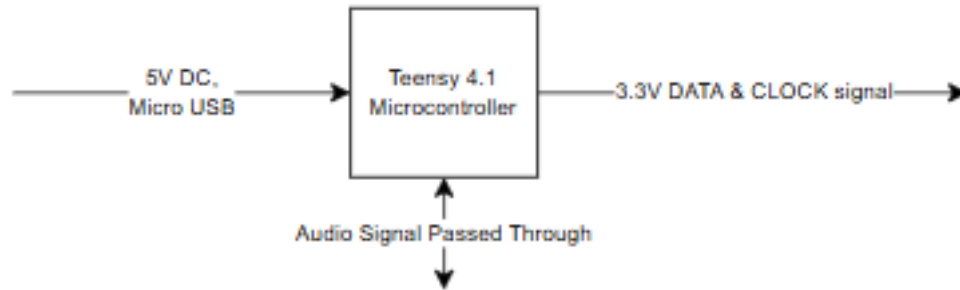


<i>Modules</i>	<i>Teensy 4.1 Microcontroller</i>
<i>Inputs</i>	5V DC Micro USB
<i>Outputs</i>	3.3V Data & Clock signal
<i>Functionality</i>	Controlling the appropriate LED to provide visual feedback on tuning.

Logic Shifter

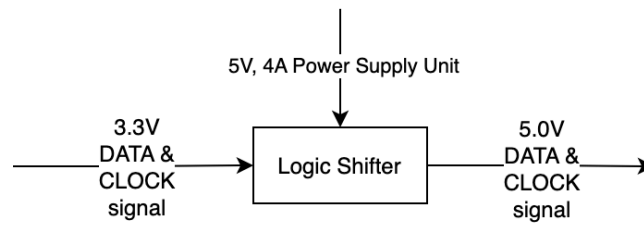


<i>Modules</i>	<i>Logic Shifter</i>
<i>Inputs</i>	3.3V Data & Clock signal, 5V/4A Power
<i>Outputs</i>	5.0V Data & Clock signal
<i>Functionality</i>	Safely translate the 3.3V logic signals from the teensy 4.1 to a higher voltage level.

Teensy Audio Shield (Rev D)

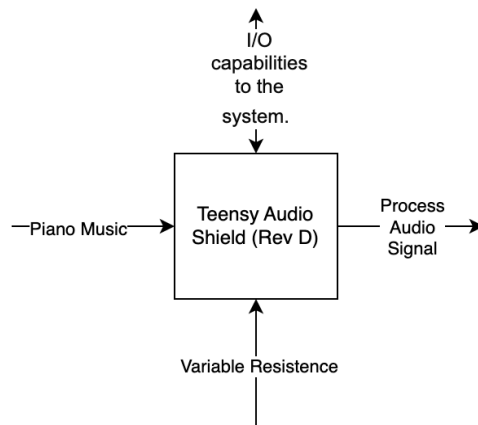


<i>Modules</i>	<i>Teensy Audio Shield (Rev D)</i>
<i>Inputs</i>	Piano Music, I/O Capabilities to the system, Variable resistance
<i>Outputs</i>	Process Audio Signal
<i>Functionality</i>	Acts as an ADC for passing digital audio to Teensy. Outputs passthrough audio to speaker, with pot for adjusting output volume.

Speaker

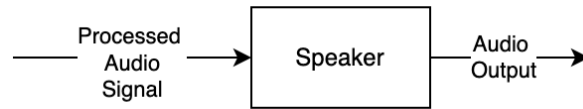

<i>Modules</i>	<i>Speaker</i>
<i>Inputs</i>	Processed Audio Signal
<i>Outputs</i>	Audio Output
<i>Functionality</i>	Provides audio passthrough of analog audio input

Potentiometer

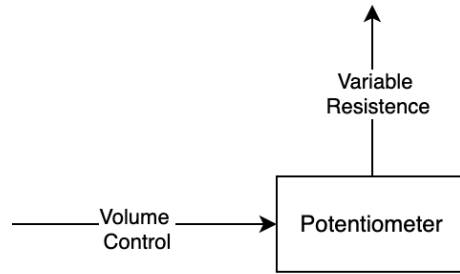

<i>Modules</i>	<i>Potentiometer</i>
<i>Inputs</i>	User input
<i>Outputs</i>	Control voltage (for audio passthrough)
<i>Functionality</i>	Acts as a variable voltage divider, allowing the microcontroller to read position by converting the mechanical rotation of its knob into an analog voltage